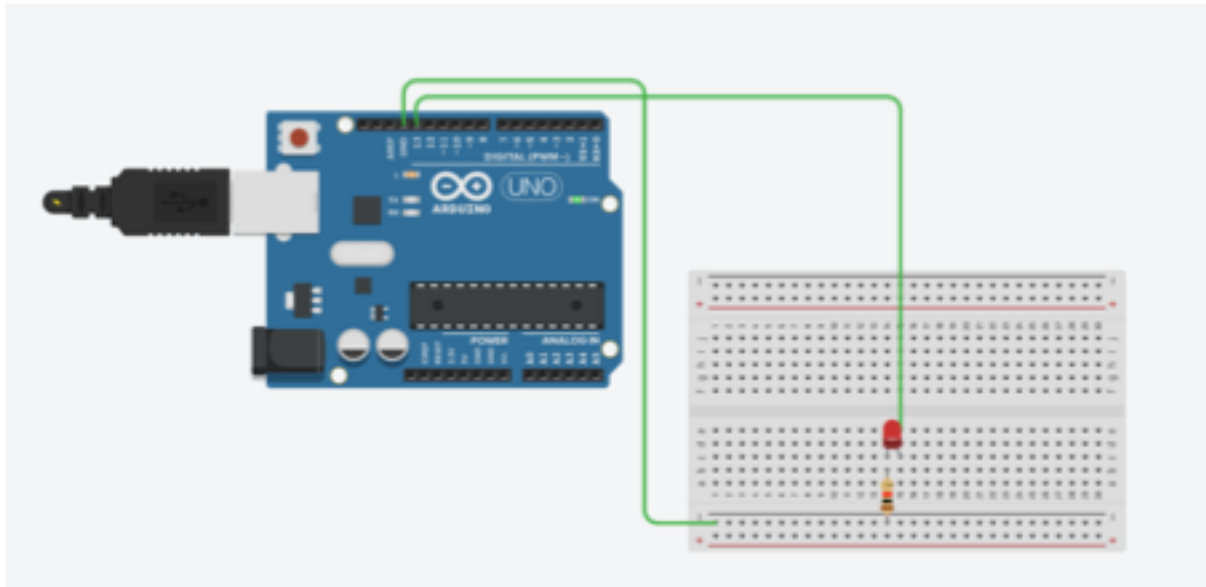


# Experiment 1:- Design a LED Flasher

## Circuit Diagram:-




## Theory:-
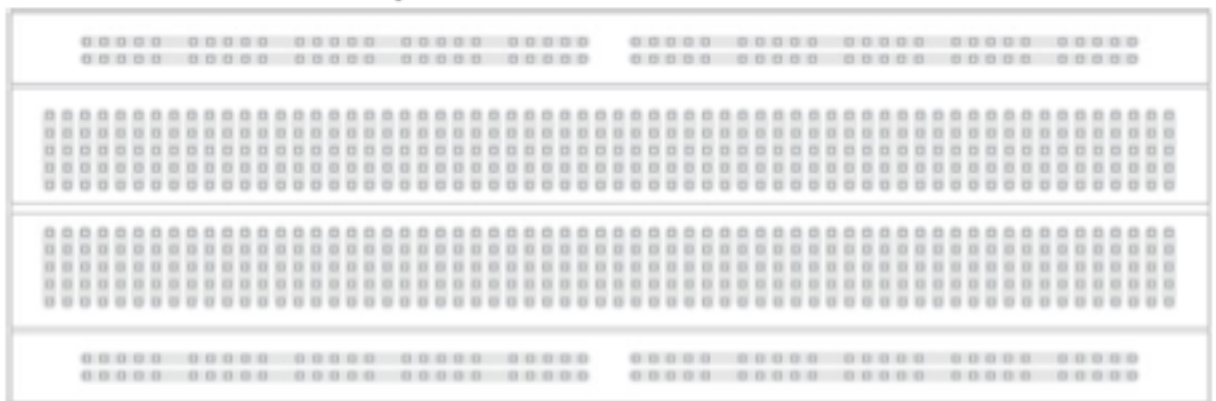
### Concept used:-

- The Arduino board can supply a power of 5V as digital output signals through the 14 pins (namely 0-13) present in it as digital input or output pins.
- The GND pin of the Arduino board acts as ground.
- In the bread board present in the above circuit diagram the two rows present at the top and bottom each, are connected with each other in series and the columns present

in between are connected in a set of 5 each.  
The connection pattern is shown below:



## **Learning and Observation:-**

### **Leanings:**

- Making a series circuit using an Arduino board and a breadboard.
- How an Arduino works and how current flows through it.
- I have now gained a practical experience of how an LED and a resistor work.

### **Observations:-**

- When we pass electrical signals to the Arduino through our code the LED blinks accordingly.

## **Problems and Troubleshooting:-**

- The LED bulb was not working . I had to replace the bulb with another one.
- The code was not uploading to the Arduino because of wrong port selection.

## **Precautions:-**

The precautions that we need to keep in mind while doing this experiment are:-

- The connections at different points should not be loose and the pins should be inserted properly.
- The two pins of the LED should be connected at their appropriate point that is, the positive point should be connected with the P pin and the negative point should be connected with the negative pin.
- We should take care that the circuit is closed .

## **Learning Outcomes:-**

- I have learned how to make circuits using an arduino board and a bread board and some other hardwares.
- Through this experiment I have gained the skill of making a circuit using different hardwares and controlling the functions done by that circuit with the help of codes.

